

Roll No.

--	--	--	--	--	--	--	--	--	--


B. Tech.
(SEM III) ODD SEMESTER EXAMINATION 2015-16
SWITCHING THEORY AND LOGIC DESIGN

[Time: 2Hrs.]

[Max Marks: 50]

Note: Attempt All Questions. All Questions carry equal marks:-

 1. Attempt any **two**: (7 x 2 = 14)
 - (a) Perform the following operation:
 - (i) $(10100111)_2 - (00110011)_2$ using 1's compliment methods.
 - (ii) Perform the addition $(-32)_{10}$ and $(29)_{10}$ using binary signed 2's compliment notation for integers. You may assume that the maximum size of integers is of 8 bits including the sign bit.
 - (iii) $(632)_{10} - (129)_{10}$ using 9's compliment.
 - (iv) Obtain the Ex-3 code and 2421 code for $(359)_{10}$.
 - (v) Obtain the Gray code and Hex code for $(59)_{10}$.
 - (vi) Implement XOR gate using minimum number of NAND gate.
 - (vii) Write even parity and odd parity for the binary eight bit data $(10010011)_2$.
 - (b) Minimize the following function by Tabular method and implement the result using NAND gate only: $F(w, x, y, z) = \sum m(1, 4, 8, 9, 13, 14, 15) + d(2, 3, 11, 12)$
 - (c) Design a combinational circuit that converts a 3-bit Gray code to a 3-bit binary number. Implement the circuit with (i) Ex-OR gate (ii) NAND gate only.
2. Attempt any **two**: (6 x 2 = 12)
 - (a) Implement the following function $F(x, y, z) = \sum m(0, 6)$ with the 2 level implementation (i) AND-NOR form (ii) NAND-AND form (iii) Or-NAND form (iv) NOR-OR form.
 - (b) Design four-input priority encoder.
 - (c) (i) Implement the following function with a multiplexer using A, B, C variables to the select lines: $F(A, B, C, D) = \sum m(0, 1, 3, 4, 8, 9, 15)$.
(ii) Implement 4-bit magnitude comparator.
3. Attempt any **two**: (6 x 2 = 12)
 - (a) Differentiate between latches and flip-flops. What do you mean by race around condition and how can overcome with this problem? Explain briefly.
 - (b) For the following state diagram obtain the state table, input equation, output equation and design the logic diagram using J-K flip-flop.



- (c) An asynchronous sequential circuit has two internal states and one output. The excitation functions and output function of the circuit are as follows:

$$Y_1 = \bar{x}_1x_2 + x_2y_1$$

$$Y_2 = x_1xy_2 + x_2$$

And output function

$$Z = x_1 + y_2$$

4. Attempt any **two**: (6 x 2 = 12)
- (a) What do you mean by counter? Design a counter that count in following sequence 0, 1, 2, 4, 5, 6, 0, 1, 2 ... using T flip-flop.
- (b) What do you mean by register? How it can be classified? Write a short note on Johnson ring counter.
- (c) Give the comparison of PROM, PLA and PAL. A combinational logic is defined by function:
- $$F_1(A, B, C) = \sum m(3, 5, 6, 7)$$
- $$F_2(A, B, C) = \sum m(0, 2, 4, 7)$$
- Implement the circuit with PLA having 3 inputs, 4 product terms and two outputs.