

B.Tech.
(SEM III) ODD SEMESTER EXAMINATION 2015-16
NETWORK ANALYSIS AND SYNTHESIS

[Time: 3 hrs.]

[Max. Marks: 100]

Note- Attempt All Questions. All Questions carry equal marks:-

- 1. Attempt any four of the following:** (5 x 4= 20)
- a) Show that the derivative of a parabolic function is a ramp function and derivative of ramp function is a step function.
 - b) With the help of mathematical expressions and characteristics curves, explain unit step, impulse and ramp signals used to analyse the network.
 - c) Define the concept of Complex Frequency.
 - d) Define the following terms:
 - i. Network analysis.
 - ii. Network synthesis.
 - iii. Complex frequency.
 - e) Synthesize the waveform as shown in **figure 1** in terms of unit and ramp functions.

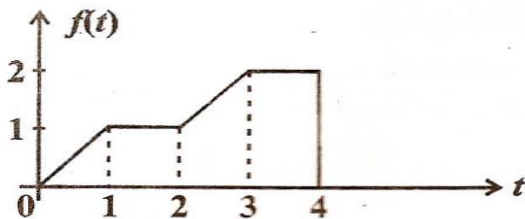


Fig. 1

- f) For the network shown in **figure 2** the switch is closed at $t=0$. If the current in L and voltage across C are 0 for $t < 0$ find $i(0+)$, $\frac{di(0+)}{dt}$ and $\frac{d^2i(0+)}{dt^2}$.

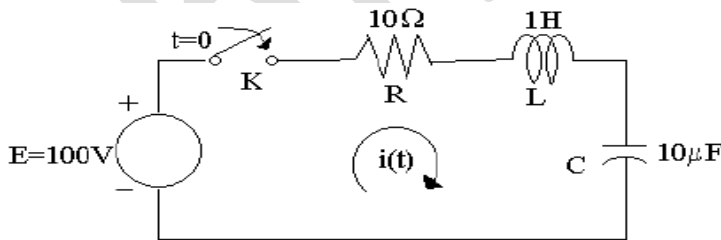


Fig. 2

- 2. Attempt any four of the following:** (5 x 4= 20)
- a) Determine the Laplace Transform of the following waveform shown in **figure 3**:

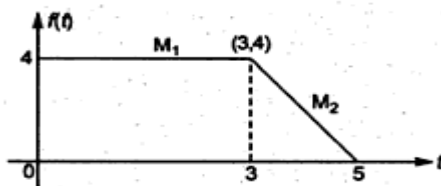


Fig. 3

- b) Find current in 4Ω resistance of **figure 4**. Using Thevenin Theorem.

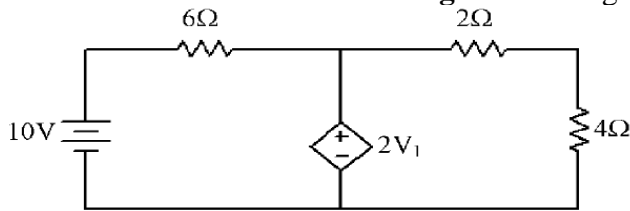


Fig. 4

- c) Represent Y-Parameter in terms of h-parameter.
 d) Find the Inverse Laplace transform of

$$X(s) = \frac{S}{(S+1)((S+2)^2+1)}$$

- e) Determine the Y-parameters of the network shown in **figure 5**:

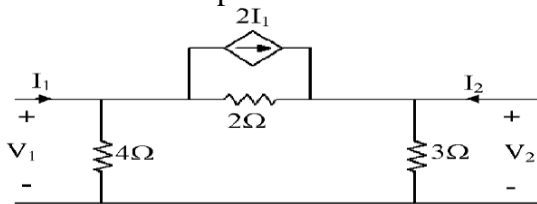


Fig. 5

- f) Prove that in a parallel-parallel interconnected two networks with admittance matrix $[Y_A]$ and $[Y_B]$ respectively, the overall Y-matrix is given as $[Y]=[Y_A]+[Y_B]$.

3. Attempt any two of the following:

(10 x 2= 20)

- a) Check the Positive Realness of the function given and give the properties of Positive Real

Function with an example : $F(s) = \frac{(s+1)(s+4)}{(s+2)(s+3)}$

- b) Check whether the polynomial is Hurwitz or not and give its properties:

$P(s) = s^7+2s^6+2s^5+s^4+4s^3+8s^2+8s+4$

- c) The driving point impedance of a one port LC network is given by $Z(s) = \frac{8(s^2+4)(s^2+25)}{s(s^2+16)}$

Obtain the First and Second Foster form of equivalent networks.

4. Attempt any two of the following:

(10 x 2= 20)

- a) Explain the term “Zero of transmission”. Realize the network function with 1Ω termination

$$Y_{21}(s) = \frac{(s+2)(s+4)}{(s+1)(s+3)}$$

- b) Enlist the properties of Transfer Function of the network. Obtain the Zero of Transmission of the

function $Z(s) = \frac{(s+1)(s+4)}{(s+2)(s+3)}$

- c) Find the Transfer Function of the network shown in **figure 6** also sketch pole-zero configuration of the network:

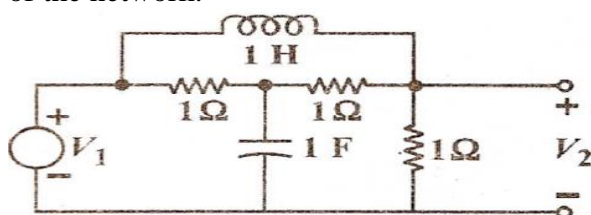


Fig. 6

5. Attempt any two of the following:

(10 x 2= 20)

- Draw the circuit of non-inverting Differentiator and Integrator using one ideal op-amp and determine its transfer function.
- Determine the value of V_O for the circuit shown in **figure 7**:

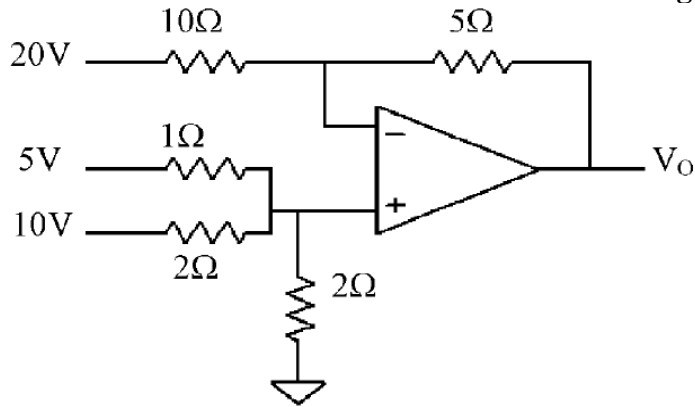


Fig. 7

- Explain Voltage Controlled Current Source and Current Controlled Voltage Source in terms of Inverting and Non-inverting Amplifier.