

Paper Code: EC-201/EC-101	Roll No. <table border="1" style="display: inline-table; border-collapse: collapse; width: 100%; height: 20px; vertical-align: middle;"> <tr> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> </tr> </table>										

B. TECH.
(SEM II) EVEN SEMESTER EXAMINATION, 2015-16
ELECTRONICS ENGINEERING

[Time: 3 hrs.]


[Max. Marks: 100]

Note: - Attempt all questions. All questions carry equal marks.


1. Attempt any four parts of the following: -

[5x4=20]

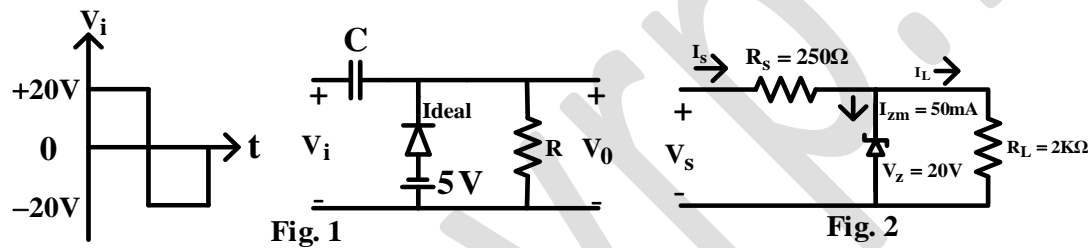- (a) Describe the difference between *n*-type and *p*-type semiconductor materials. Also give energy band diagram.
- (b) Determine the diode current at 27°C for a silicon diode with I_s 30 nA and an applied forward bias of 0.7 V.
- (c) Describe in your own words how diffusion and transition capacitances differ.
- (d) Determine V_0 for the following circuit shown in Fig. 1. Also name the configuration.



- (e) Determine the range of values of V_s for the zener diode to remain in 'ON' state. Given for zener diode $V_z=20V$, $I_{zmax}=50mA$, $R_z=0$, shown in Fig. 2
- (f) Determine V_0 for each network of Fig.3 (a) and Fig.3 (b) for the given input shown.

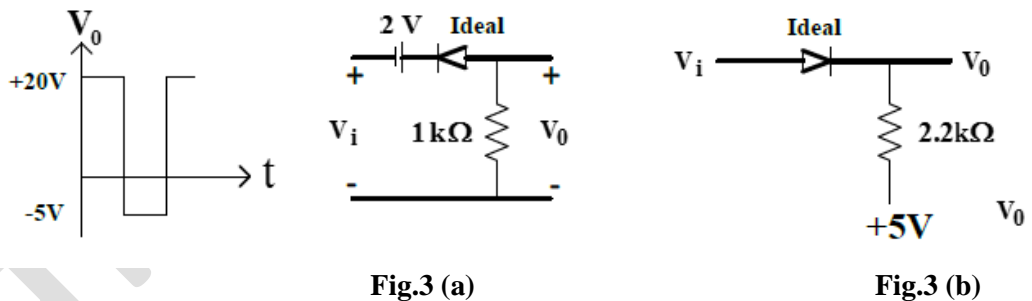

2. Attempt any four parts of the following: -

[5x4=20]

- (a) Design a clamper to perform the function indicated in Fig. 4.

