

Paper Code: EC-403

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.

(SEM IV) EVEN SEMESTER EXAMINATION, 2015-16
ELECTRONICS MEASUREMENTS & INSTRUMENTATION

[Time: 3 hrs.]**[Max. Marks: 100]****Note-** Attempt All Questions. All Questions carry equal marks.

1. Attempt any FOUR parts of the following:-

[5x4=20]

- (a) Explain gross errors, systematic errors and random errors.
- (b) The accuracies of five precision resistors are checked by comparing each of them to a 1.000 Ω . Standard resistor. The measured resistances are as follows: $R_1=1.001\Omega$, $R_2=1.002\Omega$, $R_3=0.999\Omega$, $R_4=0.998\Omega$ and $R_5=1.000\Omega$. Calculate the average measured resistance and the average deviation.
- (c) An 820 Ω resistance known to be accurate to $\pm 10\%$ carries a 10 mA current. The current was measured on the 25 mA range of an analog ammeter that has an accuracy of $\pm 2\%$ of full scale. Calculate the power dissipated in the resistor and determine the accuracy of the result.
- (d) Draw a diagram to show the basic construction of PMMC instrument. Explain the instrument operation.
- (e) A galvanometer has a 1m light-beam pointer and a coil with $N=400$, $l=d=2$ cm. the air gap flux density is $B=200\text{mT}$, and the control constant is $K=0.03 \times 10^{-6} \text{Nm/degree}$. Calculate the displacement constant, coil current when the on-scale deflection is 100 mm, and the current sensitivity.
- (f) Define the terms :
 - (i) Accuracy
 - (ii) Precision
 - (iii) Resolution
 - (iv) Threshold
 - (v) loading effect

2. Attempt any FOUR parts of the following:-

[5x4=20]

- (a) Explain the working of FET-input Voltmeter with neat diagram.
- (b) Draw circuit diagram and explain working of following AC electronic voltmeters
 - (i) Precision Rectifier voltmeter
 - (ii) Low level voltmeter
- (c) How High Voltage Probe and High Current Probe extend the ranges of measurement of multimeters. Explain with diagram.
- (d) What are various types of digital voltmeters? With a neat sketch explain the working principle of any one type of digital voltmeter.
- (e) Describe the construction and working principle of Digital Frequency Meter.
- (f) Discuss different types of Digital Multimeters.

3. Attempt any TWO parts of the following:-

[10x2=20]

- (a) Discuss briefly how Maxwell's Inductance Capacitance Bridge can be used for the measurement of unknown inductance, by providing all required derivations. Draw circuit configuration and Phasor diagram also.
- (b) Discuss the circuit diagram and working of
 - (i) *Wheatstone bridge*
 - (ii) *Q-Meter*
- (c) Write short note on:
 - (i) *Schering Bridge*
 - (ii) *Any one type of low resistance measurement method*

4. Attempt any TWO parts of the following:-

[10x2=20]

- (a) Draw the basic block diagram of an oscilloscope and explain the function of each block.
- (b) What is the role of Time Base Generator? Discuss any one type of Time Base Generator with the help of proper diagram.
- (c) Explain the working of Digital Storage Oscilloscope with the help of block diagram. Mention the advantages.

5. Attempt any TWO parts of the following:-

[10x2=20]

- (a) Sketch circuits to show how dc voltmeters and ammeters should be calibrated using standard instruments. Explain the calibration procedure.
- (b) Sketch circuits to show how dc potentiometer should be used for calibrating dc ammeters. Briefly explain.
- (c) Sketch the mechanical system of a potentiometric X-Y recorder. Explain its operation.