

EE-301

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech
(SEM III) ODD SEMESTER THEORY EXAMINATION, 2015-16
ELECTRO-MECHANICAL ENERGY CONVERSION – I

Time: 3 Hours

Maximum Marks: 100

Note: *Attempt all questions.*

Q.1. *Attempt any TWO parts of the following.* **10x2=20**

- a) Derive the expression of the voltage induced in a generic machine in generator form.
- b) Explain the concept of Energy and Co-Energy in an electro-mechanical energy conversion process.
- c) Derive the expression for the Torque in an electric motor.

Q.2. *Attempt any FOUR parts of the following.* **5x4=20**

- a) Derive the expression of induced EMF in a DC generator. What is the effect of type of winding induced EMF? Which type of armature winding is preferred for high capacity generators and why?
- b) Write in detail about armature reaction phenomenon? Explain its adverse effects.
- c) Why are Interpoles and Compensating windings used in DC machines? Explain their placement, connections and their corrective roles in DC machines.
- d) Explain how the commutation process works in a DC machine. What are faulty commutations and their disadvantages?
- e) Draw the OCC and explain the development of back emf in a DC shunt generator.
- f) Explain the External and Internal characteristics of a self excited DC generator.

Q.3. *Attempt any TWO parts of the following.* **10x2=20**

- (a) Explain whether a DC motor is self starting or not. Draw the diagram of a three point starter and explain its working. Which lacuna of three point starter is overcome by four point starter and how?
- (b) Attempt the following.
 - i) A 4 pole, separately excited wave wound DC machine with negligible armature resistance is rated for 230 volt and 5 KW at a speed of 1200 RPM. If the same armature coils are reconnected to form a lap winding, what is the rated voltage (in volts) and power in KW at 1200 RPM of the reconnected machine if the field circuit is left unchanged?
 - ii) Describe Hopkinson's test in detail.
- (c) In various speed control methods used for a DC motors, explain the sequence of events that occur to cause a change in the speed.

Q.4. Attempt any **TWO** parts of the following.

10x2=20

- a) Answer the following.
 - i) Explain how a zero voltage regulation condition is possible only for a leading power factor load in a single phase Transformer?
 - ii) Discuss about a test that is performed on two identical transformers, where the losses only are supplied by the source while keeping them fully loaded. Name the test.
- b) The maximum efficiency of a single phase, 100KVA, 1000/500 volts, 50 Hz transformer is 98% and it occurs at 80% full load, 0.9 power factor lagging. Find the efficiency at a) Full load, 0.8 power factor leading, b) 90% full load at unity power factor.
- c) Why and how are the Open circuit and Short circuit tests performed in a single phase Transformer? Why are only one type of losses considered while the other is neglected in these tests?

Q.5. Attempt any **TWO** parts of the following.

10x2=20

- (a) Explain the star-star, delta-delta, star-delta (-30 degrees) and star-delta (+30 degrees) connections in a three phase transformer.
- b) Two single phase transformers T1 and T2 each rated 500 KVA are operated in parallel. Percentage impedances of T1 & T2 are $(1+j6)$ and $(0.8 +j4.8)$ respectively. To share a load of 1000 KVA at 0.8 lagging power factor, find the contribution of T2 in KVA.
- c) Explain the excitation phenomena in single and three phase transformers.