

B.Tech.**(SEM V) ODD SEMESTER EXAMINATION 2015-16
POWER ELECTRONICS**

[Time: 3 hrs.]

[Max. Marks: 100]

Note- Attempt All Questions. All Questions carry equal marks:-**1. Answer any four parts of the following:****5x4=20**

- a) Explain the different modes of operation of SCR with the relevant characteristics.
- b) Draw two transistor model of a SCR and explain its turn-on mechanism. Why does SCR not turn-on in reverse biased condition?
- c) List specifications of a power electronic switch.
- d) List ac to dc and ac to ac power electronic converters and draw their output.
- e) Explain switching characteristics of a power transistor.
- f) Draw V-I characteristics of a GTO and explain its operation.

2. Answer any four parts of the following:**5x4=20**

- a) For type-A chopper, dc source voltage=230 V. load resistance=10 Ω . Take a voltage drop of 2 V across chopper when it is on. For a duty cycle of 0.4, calculate
 - i. average and rms values of output voltage
 - ii. Chopper efficiency.
- b) On what factors the di/dt rating of thyristor depend? What device techniques are used to improve the di/dt rating?
- c) In a series parallel connection of SCRs the voltage and current rating of a circuit are 3kV & 750A. SCRs with a rating of 800V & 175A are available. The recommended minimum derating factor is 15%. Calculate.
 - i. No. of series and parallel units required.
 - ii. R and C required for equalization if the maximum forward leakage current of SCR is 10mA and $\Delta Q=20 \mu\text{c}$.
- d) Why does unequal voltage sharing take place among series connected thyristors during steady state and dynamic state? How is equal voltage shaving obtained in both the states?
- e) Draw the circuit diagram and waveforms for resonant pulse commutation. Why the commutation capacitor in a resonant pulse commutation does get overcharged?
- f) What is dc chopper? Explain the principle of operation of a step-up chopper.

3. Answer any two parts of the following:**10x2=20**

- a) For a single phase full wave controlled converter system sketch waveforms for load voltage and load currents for:
 - i. RL load
 - ii. RLE load with free-wheeling diode across RL
- b) Draw circuit diagram of a single phase dual converter and explain its working in continuous current mode of operation. How are the firing angles of both converters decided? Discuss the need of center tapped inductor.
- c) Explain operation of a 3-phase full wave fully controlled converter feeding a highly inductive load making current continuous and draw load voltage waveform for firing angle, $\alpha > 60^\circ$. Derive an expression for dc output voltage.

4. Answer any two parts of the following:

10x2=20

- a) A single phase full wave ac regulator feeds a pure resistive load. Derive an expression for output voltage.
A single phase, 220 V, 1 KW electric room heater is connected across 220 V ac supply through a TRIAC. For a delay angle of 90° calculate the power dissipated by the heater element.
- b) A 230V, 50Hz 1phase HW rectifier is triggered at firing angle 40° . The load current extinguishes at angle of 210° find the
 - i. average output voltage
 - ii. Average load current for $R_L=25\Omega$ & $L=4\text{mH}$.
- c) Explain working of a single phase bridge type cycloconverter. Draw output voltage waveform for resistive load.

5. Answer any two parts of the following:

10x2=20

- a) Discuss the principle of working of a single phase series inverter. What are the advantages and disadvantages of series inverter?
- b) Discuss with neat circuit diagram the working of three phase bridge inverter for 180° conduction of a thyristor with three phase balanced star connected resistive load. Also state its merits and demerits.
- c) Through Fourier analysis, explain the harmonic reduction techniques and output voltage control of inverter.