

Paper Code: EEC-604

Roll No. 

--	--	--	--	--	--	--	--	--	--

**B.Tech.****SIXTH SEMESTER Back Paper EXAMINATION 2015-16  
INTRODUCTION TO ELECTRIC DRIVES****[Time: 2 Hrs.]****[Max. Marks: 50]****Note-** Attempt All Questions. All Questions carry equal marks.

- Q.1 Attempt any four parts of the following:- (2.5x4=10)**
- Draw the turn-off characteristic of an SCR and explain it.
  - Explain the working of an oscillator employing an UJT. Derive an expression for the frequency of triggering.
  - Draw and explain the equivalent circuit and V-I characteristic of the UJT in detail.
  - Justify the statement "Freewheeling diode improves the power factor of the system".
  - Describe the working of single-phase fully controlled bridge converter in the rectifying mode.
  - Draw and explain the simple SCR series inverter circuit employing class- A type commutation.
- Q.2 Attempt any two parts of the following:- (5x2=10)**
- With the circuit diagram and output voltage waveforms, explain the working of Jones chopper.
  - A chopper is operating on TRC principle at a frequency of 2 KHz on a 220 V d.c. supply. If the load voltage is 170V, compute the conduction and blocking period of thyristor in each cycle.
  - Describe the basic principle of working of a single-phase to single-phase cycloconverter for continuous conduction for bridge type cyclo-converter.
- Q.3 Attempt any two parts of the following:- (5x2=10)**
- Explain briefly the following methods of braking of a d.c. motor (i) Regenerative braking (ii) Dynamic braking.
  - Draw and explain the operation of a speed control of a d.c. series motor by a single-phase semi-converter. Draw also the associated voltage and current waveforms.
  - With the help of waveform, explain how improvement in power factor can be achieved by an asymmetrical triggering.
- Q.4 Attempt any two parts of the following:- (5x2=10)**
- Discuss the stator voltage control scheme of induction motor. Also, draw and explain speed-torque curves.
  - Explain the following terms with respect to synchronous motor (i) Pull-out torque (ii) E-curves.
  - An inverter supplies a 4-pole, 3-phase cage induction motor rated at 220 V, 50 Hz. Determine the output required of the inverter for motor speeds of (i) 900 rpm (ii) 1500 rpm.
- Q.5 Attempt any two parts of the following:- (5x2=10)**
- Explain the induction motor operation when the V/f ratio is held constant. Also, derive the expression for the maximum torque.
  - State and discuss any one method of speed control of induction motor.
  - A 80 kW, 440 V, 800 rpm d.c. motor is operating at 600 rpm and developing 75% rated torque is controlled by 3-phase, six pulse thyristors converter. If back emf at rated speed is 410 V, determine the triggering angle of the converter. The input to the converter is 3-phase, 415 V, 50 Hz a.c. Supply.