

Paper Code: EEC-401

Roll No. 

--	--	--	--	--	--	--	--	--	--

**B. Tech.**  
**(SEM. IV) Back Paper EXAMINATION, 2015-16**  
**ELECTRONIC CIRCUITS**

[Time: 3 hrs.]


[Max. Marks: 100]

**Note:-** (1) Attempt all questions.  
(2) All questions carry equal marks.


1. Attempt any four parts of the following:-

[5x4 =20]

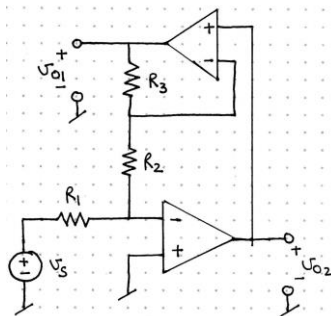(a) Find expression for the voltage  $v_{o1}$  and  $v_{o2}$  in terms of  $v_s$ ,  $R_1$ ,  $R_2$ , and  $R_3$  for the circuit in figure. The op-amps are ideal.



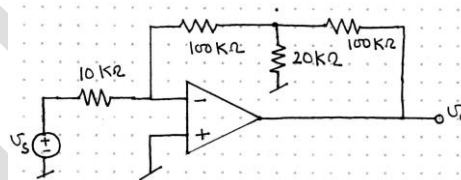- (b) Draw the integrator and differentiator circuit using op-amp and find out the transfer function.
- (c) Draw and explain the operation of three op-amps instrumentation amplifier and find the expression for the output voltage.
- (d) Describe how the performance of an op-amp is affected by the finite open loop gain of op-amp.
- (e) Find the voltage gain, input resistance and output resistance for the circuit show in figure.




(f) Using op-amp draw the practical circuits of VCCS and CCCS. Justify your answer.

2. Attempt any four parts of the following:-

[10x2 = 20]

- (a) Discuss the small signal model operation and small signal equivalent circuit model for the MOSFET.
- (b) Derive an expression for the characteristics parameters of discrete MOS common gate amplifier.
- (c) The transistor parameters are for  $M_1$ ,  $V_{TH} = +0.8V$  and  $k'_n = 40\mu A/V^2$ , and for  $M_2$ ,  $V_{TH} = -2V$  and  $k'_n = 40\mu A/V^2$  and  $W/L = 1$ . Determine the  $W/L$  ratio for  $M_1$  such that  $v_o = 0.15V$  when  $v_i = 5V$ .

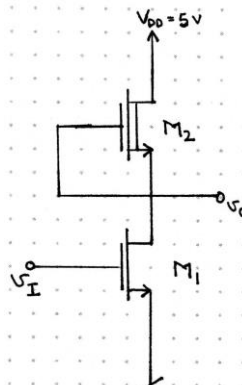


3. Attempt any four parts of the following:-

[10x2 = 20]

- (a) Discuss merits and demerits of the different types of biasing used in BJT amplifier circuits. The circuit shown in figure provides a constant current  $I_0$  as long as the circuit to which the collector is connected maintains the BJT in the active mode.

$$I_0 = \alpha \frac{V_{CC}[R_2/(R_1+R_2)] - V_{BE}}{R_E + (R_1 || R_2)/(\beta + 1)}$$

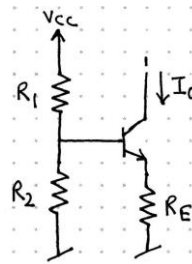

- (b) Consider a common-emitter amplifier with emitter resistance and find the expression for the amplifier input resistance, overall voltage gain, output resistance, short circuit current gain.
- (c) (i) Discuss the various internal capacitances in detail for BJT.  
 (ii) Draw the high frequency hybrid  $\pi$  model of BJT. Derive the expression given below:

$$f_T = \frac{g_m}{2\pi(C_{\pi} + C_{\mu})}$$

4. Attempt any four parts of the following:-


[10x2 = 20]

- (a) What are the merits and demerits of the differential amplifier over the single ended amplifier? Draw and explain the operation of MOS differential amplifier with a common mode input voltage and find out the range of  $v_{cm}$  over which the differential pair amplifier operates properly.
- (b) Derive an expression that show the effect on CMRR when the  $g_m$  mismatch in MOS differential amplifier.
- (c) Derive an expression for BJT differential amplifier for
- Input differential resistance
  - Differential voltage gain

5. Attempt any four parts of the following:-

[10x2 = 20]

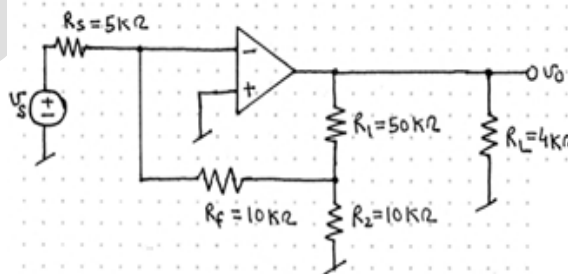- (a) Enlist the merits and demerits of the negative feedback. The op-amp in the circuit in figure has an open loop differential voltage gain of  $A_d=10^4$ . Neglect the current into the op-amp, and assume the output resistance looking back into the op-amp is zero. Determine
- The close loop voltage gain  $A_v = v_o/v_s$ .
  - The input resistance  $R_{if}$  and
  - The output resistance  $R_{of}$ .



- (b) Explain the working of a RC phase shift oscillator. Derive an expression for the frequency of oscillations. What are the merits and demerits of such oscillator?
- (c) Write a short notes on any two of the following:
- Slew rate and full power bandwidth
  - Early effect and early voltage
  - LC oscillators