

Paper Code: EE-402

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech
(SEM IV) EVEN SEMESTER THEORY EXAMINATION, 2015-16
NETWORK ANALYSIS & SYNTHESIS

[Time: 3 Hours]

[Max. Marks: 100]

Note: Attempt all questions.

1. Attempt any **TWO** parts of the following:-

[10x2=20]

- (a) Explain the following terms:
Graph, Tree, Co-Tree, Twig, Link, Oriented Graph, CutSet
- (b) Find the ranks of the following matrices taking a suitable example:
 (i) Reduced Incidence Matrix
 (ii) Basic Cutset Matrix
 (iii) Basic Tieset Matrix
- (c) Explain the concept of duality. Find the dual of the network shown in figure1.

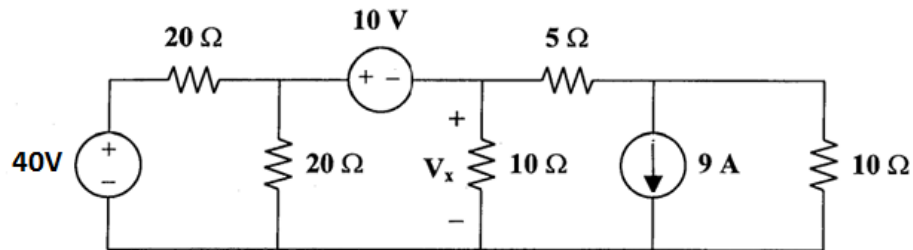


Figure 1

2. Attempt any **FOUR** parts of the following:-

[5x4=20]

- (a) Find the current I and voltage V_{ab} in figure2.

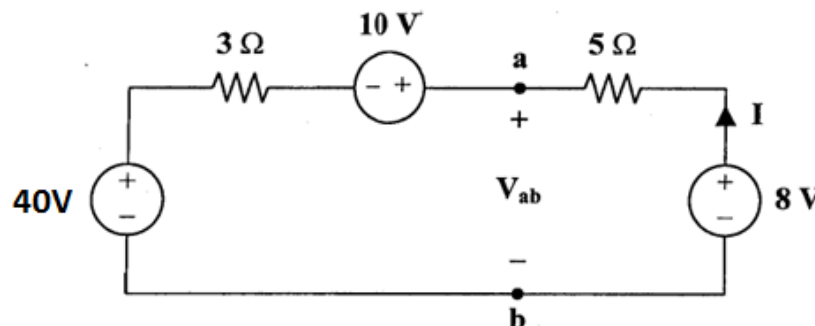


Figure 2

- (b) Derive the maximum power transfer theorem for the case when the source impedance is complex and
- (i) The load is variable with its power factor being unity.
 (ii) The load is purely reactive

- (c) State and prove the compensation theorem taking a suitable example. Where is it applied?
- (d) Assuming both voltage sources are in phase, find the value of R in fig 3 for which maximum power is delivered from circuit A to circuit B

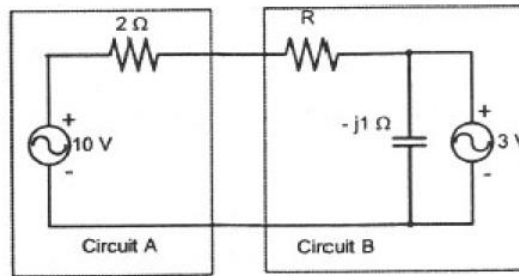


Figure 3

- (e) In the circuit shown below in fig 4, if the source voltage is $V_s = 100 \angle 53.13^\circ$, then find the Thevenin's equivalent voltage in volts as seen by load resistance R_L

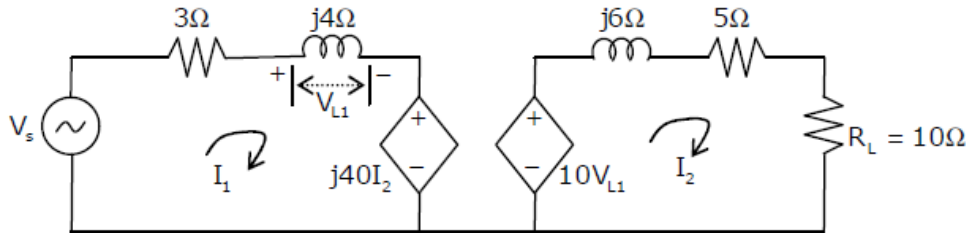


Figure 4

- (f) State and prove the Tellegen's theorem.

3. Attempt any **TWO** parts of the following:-

[10x2=20]

- (a) Find the voltage, $V_c(t)$, over the capacitor for all time $t > 0$ in fig 5.

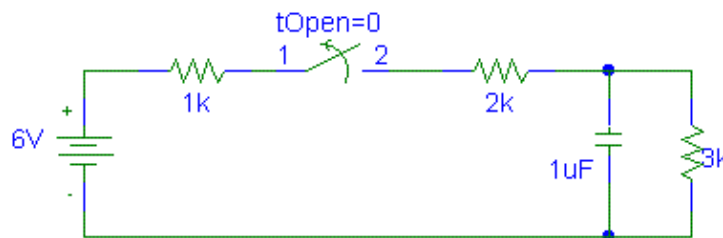


Figure 5

- (b) In the circuit shown in fig 6, given $V_c(0) = 60$ volts. Find V_c , V_x and i_0 for $t > 0$.

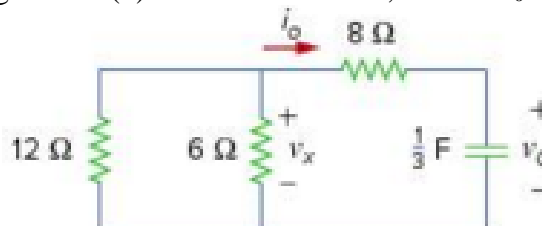


Figure 6

- (C) The switch in the circuit shown in fig7 has been closed for a long time. At $t=0$ the switch is opened. Find $i(t)$ for $t>0$.

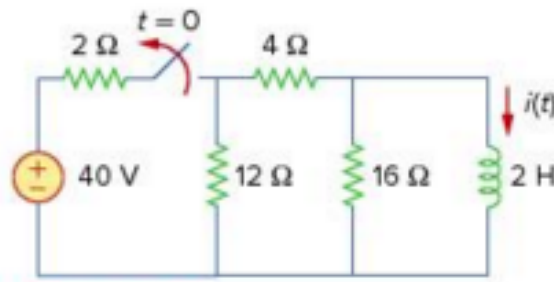


Figure 7

4. Attempt any **FOUR** parts of the following:- [5x4=20]

- Write the necessary conditions for the existence of transfer point functions giving a suitable example.
- What is meant by reciprocal and symmetric networks? Explain with the help of an example.
- Derive the condition of reciprocity and symmetry for 'h'- parameters.
- Prove that if two 2 port networks are connected in series, the Z parameter matrix of the composite two port network is the sum of the two individual Z parameter matrices.
- Find the Y and ABCD parameters of the network shown in figure 8.

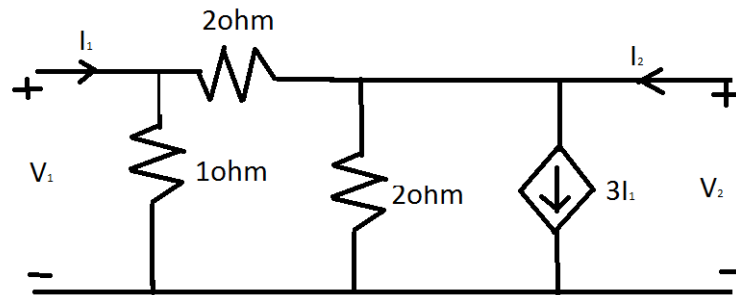


Figure 8

- Prove that the star delta conversion does not bring any change in the Z parameter matrix for the case of a resistive network.

5. Attempt any **TWO** parts of the following:- [5x4=20]

(a) Given $Y(s) = \frac{10(s^2 + 4)(s^2 + 6)}{s(s^2 + 5)}$.

Find the Foster I and Cauer II forms of network.

- Explain the properties of Hurwitz functions, LC functions, R-C and R-L functions.
- Explain the concept of positive real functions. Also explain the complete procedure to test the positive realness of a network function.