

Paper code: EE-602**Roll No.**

--	--	--	--	--	--	--	--	--	--

B.Tech.

**(SEM VI) EVEN SEMESTER EXAMINATION 2015-16
SWITCH GEAR & PROTECTION**

[Time: 3 hrs.]**[Max. Marks: 100]****Note:** Answer all five questions**1. Answer any four parts of the following:-****[5x4=20]**

- What is a zone of protection? Discuss various zones of protection in power system with the help of line diagram.
- What are the design considerations of electromagnetic relays? Also mention few of the desirable qualities of protective relays.
- Discuss about gas actuated relay in details.
- What are the functions of protective relay's. Can a relay also prevent a fault?
- What are primary and backup protection? Also compare them.
- How induction cup type construction is superior to the induction disc type?

2. Answer any two parts of the following:-**[10x2=20]**

- What is a distance relay? Draw its characteristics. How is directional features added with the over current relays? Why is it required?
- Draw the connection diagram of a differential relay for the protection. How does biasing the winding of a differential relay restricts malfunctioning of the relay against:
 - CT mismatch
 - magnetising current
- Discuss about phase comparator and amplitude comparator in detail. What are the merits of static relays?

3. Answer any two parts of the following:-**[10x2=20]**

- What is carrier current protection? For what voltage/frequency range is it used for the protection of transmission line? With neat sketches discuss the phase comparison scheme of carrier current protection
- Discuss distance protection in detail. Write short note on auto reclosing.
- How is a bus bar protected?

4. Answer any two parts of the following:-**[10x2=20]**

- A circuit breaker is rated at 1500 amps, 3000 MVA, 33 kV, 3 sec, 3-phase, oil circuit breaker. Determine the rated normal current, breaking current, making current and short time rating (current).
- Discuss the principle of arc extinction in i) an oil circuit breaker and ii) air blast circuit breaker.
- Describe with the help of a neat diagram the procedure of testing a circuit breaker in a testing station.

5. Answer any two parts of the following:-**[10x2=20]**

- With the help of neat diagram, explain construction, operating principle and advantages of SF₆ circuit breaker.
- Describe the operating principle of D.C circuit breaker. Write short notes on:
 - Current chopping
 - Interruption of capacitive current
- Give a complete protection scheme of alternator. What are the operating modes of circuit breaker?