

--	--	--	--	--	--	--	--	--	--

**B.Tech.****(SEM VII) ODD SEMESTER EXAMINATION 2015-16****DIGITAL MEASUREMENT TECHNIQUES**

[Time: 3 hrs.]

[Max. Marks: 100]

**Note- Attempt All Questions. All Questions carry equal marks:-****1. Attempt any four of the following:**

- Sketch and explain the waveform for a circuitry that is used for measurement of time interval between two events defined by  $V_H$  and  $V_L$  voltage levels.
- Explain the various techniques to measure small time interval between two events.
- Explain in brief the philosophy of digital and microprocessor/microcontroller based instruments.
- Explain Phase measurement techniques without frequency error.
- Explain why the conventional method of frequency measurement is not suitable for very frequency measurement.
- Realize a circuit & sketch voltage transfer characteristic of measuring time interval between two events represented by two voltage levels.

**2. Attempt any four of the following:**

- Explain the method for high frequency measurement.
- Draw the circuit to display the peak frequency of input signal and explain it.
- Draw the block diagram of digital frequency meter. Explain its principle of operation.
- The clock frequency of a digital counter is 1MHz. Find the value of the unknown frequency  $f$  which is measured with the same precision in the period mode as well in the frequency mode with a gating time of 2 seconds.
- Discuss a scheme for Low Frequency Measurement.
- With suitable circuit diagram show how you can measure ratio of two frequencies

**3. Attempt any two of the following:**

- Describe the methods for measurement of capacitance at high frequency.
- Explain in detail the Digital programmable Gain Amplifier. Design a programmable gain amplifier for the gains 0, -1, -2, -3, -7, choosing  $R_T = 24\Omega$ .
- Explain the working of a digital multimeter and mention its use.

**4. Attempt any two of the following:**

- Why Sample and hold circuit is considered as an essential component of modern day's instrumentation system? Explain the following terms that are associated with the problems of sample-and-hold circuits: (i) finite aperture time, (ii) signal feed through and (iii) Droop.
- Describe in detail the successive approximation method of ADC.
- Explain the input-output relationship of digital to analog converters. Discuss binary weighted charge type DACs. Justify the relation  $R_k = R/2^k$  for weighted resistor DAC.

**5. Attempt any two of the following:**

- What is the difference between VTC and VFC? Explain with the help of proper diagram. Give the detail of any single type of VTC.
- Differentiate indirect and direct type ADC and explain any one technique of direct type ADC.
- Design a 3 digit 1-V DVM based on the dual slope principle, for the following specification. Clock frequency 200 KHz, conversion rate 25 samples/s, auto-ranging arrangement for 1, 10, 100, 1000V ranges, independent of 50Hz hum present in the signal,  $R_{in} = 10 M\Omega$ .