

Paper Code: MEC 918

Roll No.

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

M.Tech.
(SEM III) ODD SEMESTER EXAMINATION 2015-16
Electronic Systems Design

[Time: 3 hrs.]

[Max. Marks: 100]

Note- Attempt All Questions. All Questions carry equal marks:-**1. Attempt any FOUR of the following questions:**

- (a) What is SNR? Why should we improve the SNR?
- (b) Write short note on:
 - (i) Parameters involved in PCB design
 - (ii) CAD for PCB design.
- (c) Explain the need of using anti-aliasing filters in the process of signal conditioning.
- (d) List some software available to draw the PCB layout. What are the limitations of PCB design?
- (e) Define CMRR of an op-amp. Determine the output of op-amp for input voltage of 300 μ V and 240 μ V. the differential gain of the amplifiers is 5000 and the value of CMRR is 100000.
- (f) Design a second order low-pass filter for a cutoff frequency of 1KHz and passband gain of 1.587.

2. Attempt any FOUR of the following questions:

- (a) Explain the PCB design rules and its limitations for power electronics circuits.
- (b) Discuss all the steps involved in conversion of analog data into digital data.
- (c) Explain working of MOSFET as a switch. Draw the circuit diagram for NMOS logic inverter, PMOS logic inverter and CMOS logic inverter.
- (d) Discuss in brief the transfer functions of Butterworth filter, Chebyshev filter and Bessel filter.
- (e) Explain the working of smoothing filters?
- (f) Write short note on:
 - (i) Isolation Amplifier
 - (ii) Switched Capacitor circuits

3. Attempt any TWO of the following questions:

- (a) What is an Instrumentation Amplifier and what is its role in instrumentation? Draw the scheme of connections and derive the expression for its gain.
- (b) Explain the interfacing of ADC and DAC with the DSP.

- (c) Why grounding and shielding is needed in digital systems? Give general recommendations for low-noise design procedure with sensor characteristics fixed.

4. Attempt any TWO of the following questions:

- (a) Design a second order low pass filter.
- (b) Explain spectral characteristics of noise. What are different types of noise? Explain below noise types in detail:
- (i) Thermal noise
 - (ii) Shot noise
 - (iii) $1/f$ noise
- (c) Determine the rms thermal noise voltage of resistance of 1K, 50 K, 1 M for each of the following noise B.W. 50 KHz, 1 MHz, 20 MHz. Consider $T=290K$.

5. Attempt any TWO of the following questions:

- (a) What do you mean by signal averaging? Derive an expression for the improvement signal to noise ratio for n samples.
- (b) Explain the advantage /disadvantages of serial interfacing over Parallel interfacing with microcontroller.
- (c) Explain following DAC characteristic:
- I. Resolution
 - II. Maximum sampling rate
 - III. Monotonicity
 - IV. Total harmonic distortion and noise
 - V. Dynamic rang