

Paper Code: MEC-930	Roll No.
----------------------------	---

M.Tech.
(SEM II) EVEN SEMESTER EXAMINATION, 2015-16
TESTING & VERIFICATION of VLSI CIRCUITS

[Time: 3 hrs.]


[Max. Marks: 100]

Note- Attempt All Questions. All Questions carry equal marks.

- Q.1.** Attempt any **TWO** parts of the following. [10x2=20]
- (a) What do you mean by testability of VLSI circuits? Why is verification of VLSI circuits required? Explain the testing mechanism.
 - (b) Explain the different kinds of physical faults that can occur in a CMOS chip, and relate to typical circuit failure.
 - (c) What is fault simulation? What are the different fault simulation techniques? Discuss each of them.

- Q.2.** Attempt any **TWO** parts of the following. [10x2=20]
- (a) Explain the terms :
 - (i) Test and Testability (ii) System partitioning (iii) Test coverage (iv) Functionality tests.
 - (b) Discuss in detail the Bridging Fault Model and Delay Fault Model. Explain with suitable examples.
 - (c) Draw two inputs CMOS NAND gate. Find and explain what are the different possible single stuck at fault also compare the output for each case with fault free.. If a bridging exists between the source and drain at one of the driver transistor, find the conditions of input for average output.

 - Q.3.** Attempt any **TWO** parts of the following. [10x2=20]
- (a) Find the primitive D-Cube for two input NOR gate for output Z: s-a-1. Use D- algorithm to generate test vectors for d: s-a-0 in the circuit shown in figure.



- (b) What do you mean by sensitized path? Describe the method of sensitized path based testing. Using sensitized path technique, find the test pattern to detect the fault d: s-a-0 and d: s-a-1 in the circuits shown in Figure.

- (c) Explain Boolean difference method for test generation. Use Boolean difference method to generate test vectors for single stuck at fault at e: s-a-1 and e: s-a-0 faults in the circuit shown in Figure

Q.4. Attempt any **TWO** parts of the following. **[10x2=20]**

- (a) What do you mean by DFT? Why is it needed? Explain with example, how controllability and observability of a circuit under test can be improved?
- (b) How scan design techniques are used to test sequential circuit? Explain the working of the scan chain based technique with necessary circuit diagram.
- (c) Draw the architecture of boundary scan test (BST) and explain the operation. Why is BST required?

Q.5. Write short notes on any **TWO** of the following. **[10x2=20]**

- (a) Built-in Logic Block Observer (BILBO)
- (b) Ad-hoc Testing
- (c) Physical Verification
- (d) Level Sensitive Scan Design (LSSD)