

Paper Code: EC302

Roll No.

--	--	--	--	--	--	--	--	--	--

**B.TECH**  
**(SEM III) ODD SEMESTER EXAMINATION 2016-17**  
**SWITCHING THEORY AND LOGIC DESIGN**

[Time: 2 hrs.]

[Max. Marks: 50]

Note- Attempt All Questions. All questions carry equal marks:-

**1. Attempt any FOUR questions of the following:-****(3.5 X 4 = 14)**

(a) Simplify the following expression using K-map:

$$F(A, B, C, D) = A \cdot B (C \oplus D) + \bar{A} \cdot B (C \odot D) + C \cdot D (A \oplus B) + \bar{C} \cdot D (A \oplus B)$$

(b) Design a BCD to Excess-3 converter.

(c) Implement the following function with a multiplexer using A, B, C variables to the select lines:  $F(A, B, C, D) = \sum m(0, 1, 3, 4, 8, 9, 15)$ .

(d) Convert the RS flip flop to JK flip flop showing all the steps of conversion.

(e) Design a 4-Bit magnitude comparator.

(f) Find the minimal SOP for the following Boolean expression using Quine-Mc-Cluskey method.

$$F(A, B, C, D) = \sum m(1, 2, 3, 7, 8, 9, 10, 11, 14, 15)$$

 
**2. Attempt any TWO questions of the following:****(6 X 2 = 12)**(a) By means of a timing diagram show the signals of the outputs X, Y and Z in Fig. 1, as a function of the two inputs A and B for all combinations. If the propagation delay of one gate is  $5\mu s$  then, what will be the propagation delay of output Z?

Fig.1

(b) Design a 3 bit up/down ripple counter.

(c) Design a combinational circuit using a ROM that accepts a 3-bit number and generates an output binary number equal to the square of the input number.

(d) Design a combinational circuit that converts a 3-bit Gray code to a 3-bit binary number. Implement the circuit with (i) Ex-OR gate (ii) NAND gate only.

**3. Attempt any THREE questions of the following:****(4x3 = 12)**

(a) Distinguish the difference between Mealy and Moore models. Explain with a relevant example. Identify the type of circuit is shown in Fig. 2? Draw state diagram of this.

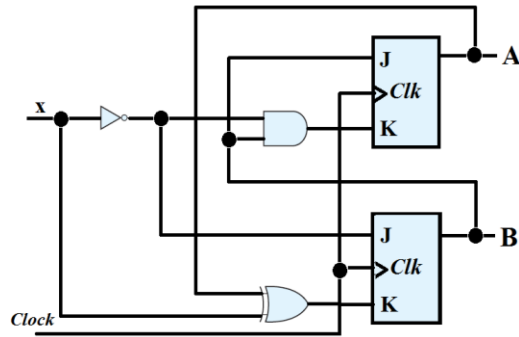


Fig.2

- (b) Define Hazards? Explain different types of Hazards with proper example. Also discuss the methods by which it can be removed.
- (c) Implement a Universal shift register with suitable diagram.
- (d) Describe the basic properties of 4-bit Ring counter and Johnson counter.

4. Attempt any TWO questions of the following:

(6 X 2 = 12)

- (a) Implement the following function in PLA

$$F_1(A,B,C) = \sum(0,1,2,4)$$

$$F_2(A,B,C) = \sum(0,5,6,7)$$

- (b) Reduce the state diagram shown in the Figure 3 and assign state using one shot scheme. What are the advantages of one hot scheme over general binary assignment?

 


Fig.3

- (c) Design a synchronous counter which repeats the following binary equivalent sequence of decimal numbers- 0, 2, 4, 6.
- (d) For the following state diagram obtain the state table, input equation, output equation and design the logic diagram using J-K flip-flop.
- (e)

