

Paper Code: EC-309

Roll No.

--	--	--	--	--	--	--	--	--	--

B. TECH.
THIRD SEMESTER EXAMINATION, 2016-17
DIGITAL LOGIC DESIGN

[Time: 3 hrs.]

[Max. Marks: 100]

Note:- Attempt All questions. All questions carry equal marks.

1. Attempt any *four* parts of the following: -

[5x4=20]

- (a) Perform the arithmetic operations $(+42) + (-13)$ and $(-42) - (-13)$ in binary using the signed-2's complement representation for negative numbers.
- (b) Simplify the following function with Karnaugh-map (K-map) and implement using NOR gates only: $F(x, y, z) = \sum m(0, 2, 6)$.
- (c) Simplify the following function and implement with two-level NAND gate circuit:
 $F(A, B, C, D) = BD + BC\bar{D} + A\bar{B}\bar{C}\bar{D}$
- (d) Simplify the following Boolean function in (a) sum of products and (b) product of sums: $F(A, B, C, D) = \sum m(0, 1, 2, 5, 8, 9, 10)$
- (e) Find the minterms of the following Boolean expressions by first plotting each function in a map: $F(w, x, y, z) = wxy + \bar{x}\bar{z} + \bar{w}xz$
- (f) Simplify the following Boolean function using the tabulation method:
 $F(A, B, C, D) = \sum m(0, 1, 2, 8, 10, 11, 14, 15)$

2. Attempt any *four* parts of the following: -

[5x4=20]

- (a) Design an 8-bit parallel binary adder to add A and B.
Where $A = 10110101$, $B = 11001101$. (Show with proper labeling)
- (b) Implement a full subtractor using 3 to 8 line decoder.
- (c) Design a BCD adder to add $(20)_{10}$ and $(12)_{10}$.
- (d) Design a BCD to excess-3 code converter using various logic gates.
- (e) Design a 4-bit binary magnitude comparator showing output $y=1$ when both numbers A and B are equal and $y=0$ otherwise.
- (f) Implement a full adder using 4x1 multiplexers.

3. Attempt any *two* parts of the following: -

[10x2=20]

- (a) (i) Design 4-bit switch-tail ring counter using D flip-flops.
(ii) Design Mod-6 gray code counter using J-K flip-flops.
- (b) Draw and explain 4-bit Parallel In Serial Out (PISO) shift left register using D flip-flops.
- (c) Draw the BCD ripple counter. Also explain with timing diagram.

4. Attempt any *two* parts of the following: -

[10x2=20]

- (a) Explain race-around condition in detail. Give the remedy to remove it using gate level diagram.
- (b) Design a sequential circuit having three flip-flops A, B and C, one input, x and one output y for the following state diagram (fig.1). The circuit is to be designed by treating the unused states as don't-care conditions. (Use D flip-flops in the design)

 


Fig.1

- (c) Perform the state reduction for the given state diagram (fig.2) by deriving its state table. Also draw the reduced state diagram.

 


Fig.2

5. Attempt any *two* parts of the following: -

[10x2=20]

- (a) Explain hazards in detail. Find a circuit that has no static hazards and implement the Boolean function: $F(A,B,C,D) = \sum m(0,2,6,7,8,10,12)$
- (b) Design a combinational circuit using a ROM. The circuit accepts a 3-bit number and generates an output binary number equal to the square of the input number.
- (c) A combinational circuit is defined by the functions
 - $F_1(A, B, C) = \sum m(3, 5, 6, 7)$
 - $F_2(A, B, C) = \sum m(0, 2, 4, 6)$
 Implement the circuit with PLA, PAL and PROM.