

Paper Code: EC-501

Roll No. 

--	--	--	--	--	--	--	--	--	--

**B.Tech.**  
**(SEM V) ODD SEMESTER EXAMINATION 2016-17**  
**INTEGRATED CIRCUITS**

*Time: 3 Hours**Maximum Marks: 100***Note:** *Attempt all questions. All questions carry equal marks***Q.1. Attempt any four parts of the following****5x4**

- (a) Draw and find out  $R_{in1}$ ,  $R_{out1}$  and  $G_{m1}$  of input stage of 741 Op-amp?
- (b) Explain the advantage of improved Wilson MOS current mirror circuit and derive the expression of  $R_{out}$ ?
- (c) Draw and explain the advantage of Widlar current mirror circuit.
- (d) Enlist the five applications of Analog Multiplier.
- (e) Derive the mathematical expression for equivalent impedance for inductance simulators.
- (f) Explain the working operation of CMOS inverter with VTC characteristics.

**Q.2. Attempt any two parts of the following****10X2**

- (a) Draw and explain basic current mirror circuit also express relation between  $I_{ref}$  and  $I_o$  when we consider effect of  $\beta$ , junction area ratio ( $m$ ) and early effect?
- (b) Give the transfer function of second order band pass filter with center frequency of  $10^5$  rad/sec, a center frequency gain of 10 and 3db bandwidth of  $10^3$  rad/sec.
- (c) Draw & explain Triangular Wave Generator with necessary waveforms also find out time period of oscillation?

**Q.3. Attempt any two parts of the following****10X2**

- (a) (i) Design a second order low pass filter of cut-off frequency 2 KHz.  
(ii) Derive the all possible transfer function for state variable filter.
- (b) The timer IC 555 is used as astable multivibrator. It is desired to have square wave output with 50% duty cycle of 2 KHz. The timing capacitor is of 0.01 f. Find the values of resistors required and draw the circuit.
- (c) Explain block diagram of PLL. Define and derive expression for Capture range and Locked range and plot variation in input control voltage of VCO with incoming frequency?

**Q.4. Attempt any four parts of the following**

**5X4**

- (a) Explain Full wave Precision Rectifier with its transfer characteristic.
- (b) Determine feedback voltage, period and frequency in the below figure 1

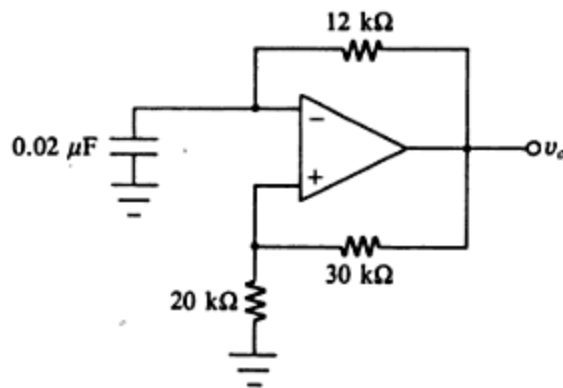


Figure 1

- (c) Find Differential Gain of the circuit as shown in figure 2

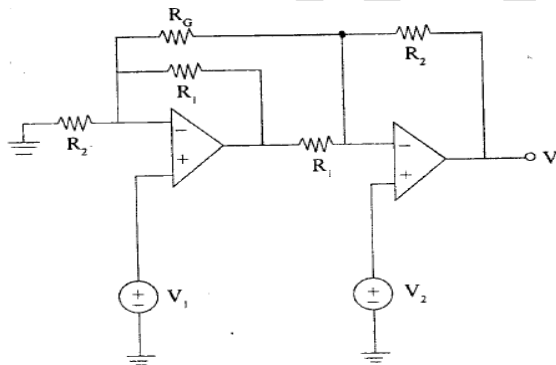


Figure 2

- (d) Explain peak detector with input and output waveforms.
- (e) Draw the circuit of a log-amplifier and explain its working.
- (f) Implement Clocked SR Flip Flop using CMOS technology with NOR logic gate.

**Q. 5. Attempt any four parts of the following**

**5X4**

- (a) Draw the circuits of Instrumentation Amplifier and find out overall differential gain  $A_d$ .
- (b) Draw and explain linear phase detector using Ex-OR and find out relation between  $\tau$  and phase difference.
- (c) Explain Binary Weighted type Digital to Analog Converter.
- (d) Draw and explain KHN Biquad Filter.
- (e) Draw the D-Flip Flop using CMOS and explain its Master slave configuration.
- (f) Design a two input CMOS logic circuit EX-OR gate.