

Paper Code: EC-101	<table border="1" style="width: 100%; height: 20px; border-collapse: collapse;"> <tr> <td style="width: 10%; text-align: center;">Roll No.</td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> <td style="width: 5%;"></td> </tr> </table>	Roll No.									
Roll No.											

**B.TECH
(SEM I) ODD SEMESTER EXAMINATION 2016-17
BASIC ELECTRONICS ENGINEERING**


[Time = 3 Hr]

[Max. Marks: 100]

Note: 1. Attempt all the question all the questions are compulsory
2. Assume the data if required in any questions.

Q.1. Attempt any four of the following questions: (4x5=20)

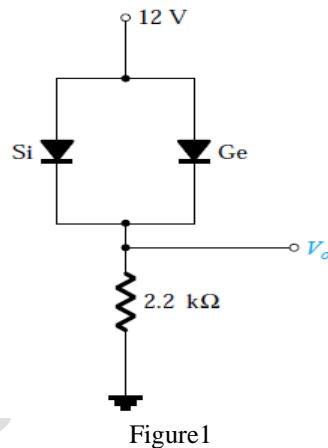- a) Differentiate among conductor, insulator and semiconductor using energy band concept. Also describe the difference between *n-type* and *p-type* semiconductor materials.
- b) Differentiate between Transition capacitance and diffusion capacitance of a p-n junction diode.
- c) What is the **zener** breakdown mechanism also write the comparison of **zener** diode and p-n junction diode
- d) Draw the CE npn transistor configuration and its characteristics show cut-off, saturation, and active region. Also prove that : $I_c = (1+\beta)I_{CO} + \beta I_B$
- e) Define and explain the parameter trans-conductance g_m , drain resistance r_d and amplification μ of a JFET. In JFET $I_{DSS}=8mA$, $V_P = -4V$ biased at $V_{GS} = -1.8V$. Determine the value g_m
- f) Determine the voltage V_o for the network of Figure 1



Q.2. Attempt any two of the following questions: (2x10=20)

- a) Determine V_o for each network of Figure 2.

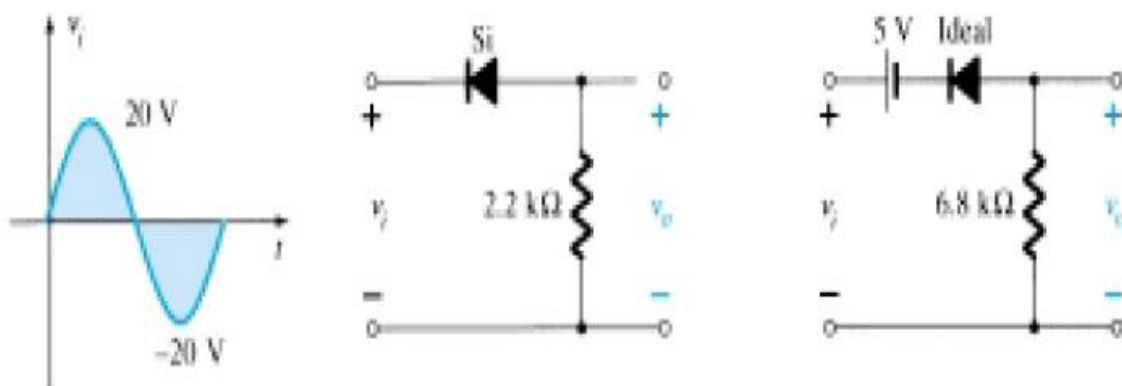


Figure 2

- b) Sketch V_o for each network of Fig 3.

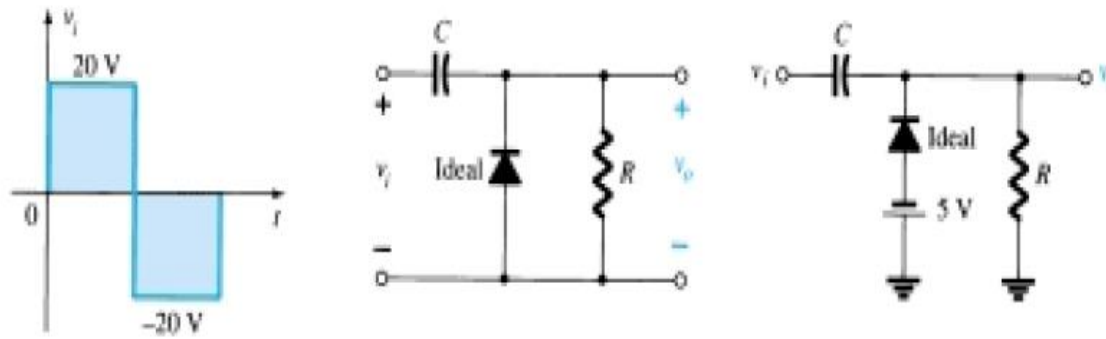


Figure3

c) Determine the minimum value of R_L to ensure that the Zener diode is in the “on” state in Figure 4.

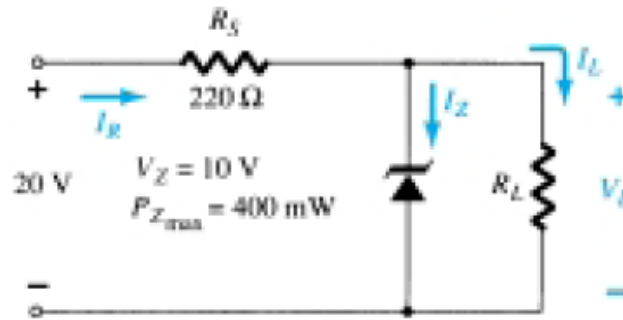


Figure 4.

f) Explain the working of a **voltage doubler** with neat diagram

Q.3. Attempt any two of the following questions:

(2x10=20)

- (a) Explain ant type of MOSFET with diagram and draw the transfer and output characteristics.
- (b) (i) Explain the principle of operation of JFET with neat diagram. Also sketch its transfer and output characteristics.
- (ii) For voltage divider configuration as shown in Figure 5, if $V_D = 12V$ and $V_{GSQ} = -2V$, determine the value of source resistance (R_S).

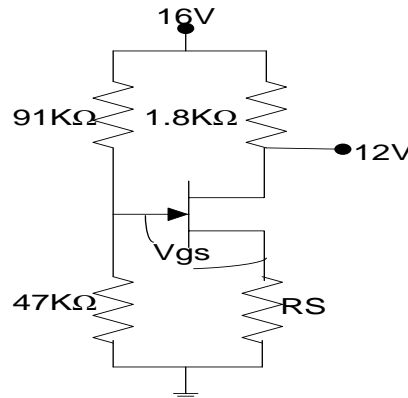


Figure 5

(c) For the emitter bias network of Figure 6, determine:
 (a) I_B . (b) I_C . (c) V_{CE} . (d) V_C . (e) V_E . (f) V_B . (g) V_{BC} .

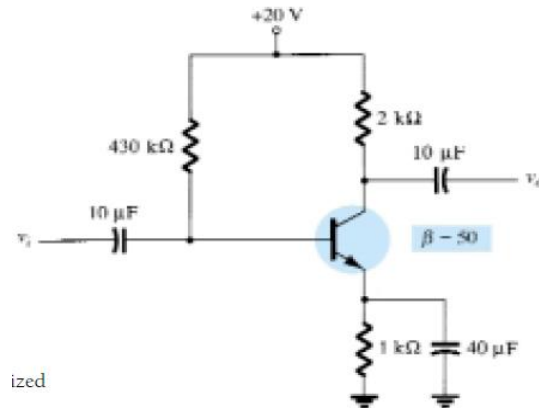


Figure 6

Q.4. Attempt any two of the following questions.

(2x10=20)

- (a) Enlist the ideal characteristic of Op-amp and Explain the following terms Slew rate & CMMR. An operational Amplifier has a differential gain of 10^3 and a CMRR of 100, input voltages are $120\mu\text{V}$ and $80\mu\text{V}$. Determine the output voltage.
- (b) Find out the voltage of the following circuit as shown in Figure 7.

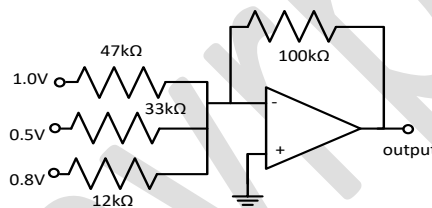


Figure 7

- (c) Determine the output voltage V_{out} assume that $V_1=2\text{V}$ and $V_2 = 4\text{V}$ as shown in Figure 8.

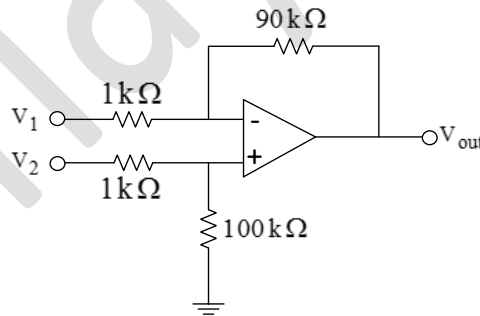


Figure 8

Q.5. Attempt any two of the following questions:

(2x10=20)

- (a) What are the basic constructional differences between a Varactor diode and a Tunnel diode? Explain briefly the operation and characteristics of a tunnel diode.
- (b) Define light emitting materials. What determines the emission of colour of LED? Describe the working of solar cell. What are the applications of these devices?
- (c) (i) Explain the operation and characteristic of silicon controlled rectifier. Also describe the application of the SCR.
(ii) Explain the working of a **full wave voltage doubler** with neat diagram