

Paper Code:EE-701

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.
SEVENTH SEMESTER EXAMINATION, 2016-17
FLEXIBLE AC TRANSMISSION SYSTEMS

[Time: 2 hrs.]

[Max. Marks: 50]

Note: Attempt ALL questions. Assume suitable data, if required. All question carry equal marks.

1. Answer any *FOUR* parts of the following:- **(3.5x4=14)**
 - (a) Explain the power flow and dynamic stability considerations of a transmission interconnection.
 - (b) Explain in detail about the classification of different FACTS controllers.
 - (c) Explain what is meant by TCSC and UPFC.
 - (d) Explain the benefits from FACTS technology.
 - (e) State the salient features of UPFC.

2. Answer any *TWO* parts of the following:- **(6x2=12)**
 - (a) Explain the working and characteristic of thyristor controlled and thyristor switched reactor.
 - (b) Explain the effect of shunt compensation on transient stability and power oscillation damping.
 - (c) Explain the working and characteristics (V-I and loss versus var output) of fixed capacitor, Thyristor-Controlled Reactor Type Var Generator.

3. Answer any *TWO* parts of the following:- **(6x2=12)**
 - (a) Explain in detail about series capacitive compensation and voltage stability in transmission lines.
 - (b) Explain the working and impedance vs. delay angle characteristic of TCSC.
 - (c) Explain the current and voltage waveforms of the TCSC operated in the capacitive and inductive region.

4. Answer any *TWO* parts of the following:- **(6x2=12)**
 - (a) Compare the V-I, V-Q characteristics and transient stability of STATCOM and SVC.
 - (b) Explain the basic operating principle and basic control approach of STATCOM.
 - (c) Explain in detail about Static synchronous series compensator with transmitted power versus transmission angle characteristics.