

Roll

--	--	--	--	--	--	--	--	--	--

Paper Code: IC-703

B.TECH
(SEM VII) ODD SEMESTER EXAMINATION 2016-17
DIGITAL MEASUREMENT TECHNIQUE

[Time: 3 hrs.]

[Max. Marks: 100]

Note- Attempt All Questions. All questions carry equal marks.

1. Attempt any **FOUR** parts of the following:- (5 X 4 = 20)

- (a) What is the need of digital measurements? Explain the generalized schematic for measuring any physical quantity.
- (b) If the main and Vernier oscillator have time periods of 10.06 and 10.001 μs , respectively, and the time interval to be measured is 1410.05 μs , what would be the main and the Vernier counter reading? Find the total measurement time.
- (c) Describe the Vernier technique for small time interval measurement with the help of Block diagram and waveforms.
- (d) Explain the working principle of a circuit with drawing waveform for measurement of time interval without any priority.
- (e) How the circuit shown in Fig.1, works as a periodic time measuring circuit? Explain with proper waveforms of C, G, V_o and Q.

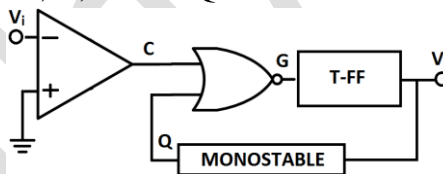


Fig.1

(f) Describe the capacitance measurement technique using a Schmitt trigger.

2. Attempt any **TWO** parts of the following:- (10 X 2 = 20)

- (a) Derive the counter reading for power system frequency deviation technique and discuss the problem which may occur in this technique. Explain with the help of circuit diagram and waveforms.
- (b) What is the need of peak frequency measurement? Explain peak frequency measurement technique with proper diagram.
- (c) How the circuit shown in Fig.2 is utilized in average frequency deviation measurement? Explain with proper steps. Also suggest a circuit to detect the higher and lower frequency among f_1 and f_2 .

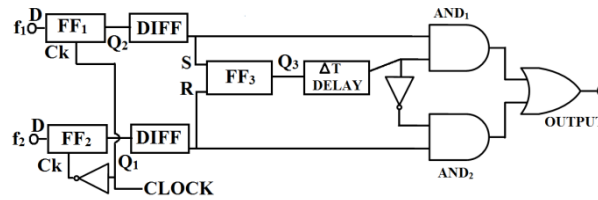


Fig.2

3. Attempt any **TWO** parts of the following:- (10 X 2 = 20)

- (a) Multiple gains amplifier can be designed through MUX and IC-741 for digitally programmed input, than what is the basic need of Programmable gain Amplifiers? Explain with example. Design a PGA for gains 1, 2/3, 1/3, 2/3.
- (b) Explain basic principal of programmable Biquad. How the stray capacitance can be eliminated by this scheme?
- (c) What do you understand by single mode and multimode switching in digitally programmable consistor designing? Prove that for single mode switched S-ladder network the value of R_k is given by:

$$R_k = \begin{cases} \frac{|A_k| - |A_{k-1}|}{g}, & 2 \leq k \leq N \\ \frac{|A_1|}{g}, & k = 1 \end{cases}$$

4. Attempt any **TWO** parts of the following:- (10 X 2 = 20)

- (a) What are the advantages of DACs designed from PGA realizations? Realize 2-Bit inverting and non-inverting DACs with minimum number of components making use of PGAs.
- (b) What type of switches can be utilized in designing DACs? Explain Bipolar transistor used in inverse mode as a switch.
- (c) Realize a 7-bit two stage DAC with a minimum spread in R-values. Compare the spread and total resistance with those of single stage DACs.

5. Write Short notes on any **Two** of the following parts:- (10 X 2 = 20)

- (a) VTC (Voltage to Time Converter)
- (b) VFC (Voltage to Frequency Converter)
- (c) Sampling, Time Division Multiplexing, and Quantization.