

--	--	--	--	--	--	--	--	--	--	--	--

MCA
(SEM I) CARRY OVER EXAMINATION 2016-17
DIGITAL LOGIC DESIGN

[TIME: 3 hrs]

[Max. Marks: 70]

Note: Attempt all questions. All questions carry equal marks.**Q.1.** Attempt any TWO of the following:

- What do you understand by the digital logic? How digital logic design is helpful in understanding computer system.
- Perform the following operation.
 $(738)_8 - (123)_{16} + (100)_{10}$
- Perform the following subtraction using (i) 1's complement and (ii) 2's complement
 $(11010)_2 - (10000)_2$
 $(1000100)_2 - (1010100)_2$

Q.2. Attempt any TWO of the following:

- What is the role of error correcting codes? Explain any two types of error correcting codes with example.
- What is gray code? Why it is called unit distance code? Find the gray codes for the following binary members
(i) 11001100 (ii). 01011110
- Simply the following Boolean equations using Boolean algebra rules.
(i). $Y(A, B, C) = ABC + A\bar{B} + ABC\bar{C}$
(ii). $Y(A, B, C, D) = ACD + \bar{A}BCD$

Q.3. Attempt any TWO of the following:

- What do you understand by standard representation for logical function-
(i). Sum of Products (ii). Product of Sum
- Minimize the following expressions using K-map
(i). $Y(A, B, C) = \sum m(0, 1, 2, 3, 4, 5, 6, 7)$
(ii). $Y(A, B, C) = \sum m(0, 2, 4)$
- Design a combinational logic circuit with four input variables that will produce logic 1 output when the number of 1s in the inputs is even.

Q.4. Attempt any TWO of the following:

- Draw and explain n-bit parallel adder.
- What do you understand by Mod of counter? Draw Mod-5 up counter & explain its working.
- What do you understand by multiplexor? Why it is called data selector. Draw a 16x1 multiplexor and explain its working.

Q.5. Write short note on any two of the following:

- Bidirectional shift register.
- Algorithm state machines.
- Programmable logic devices.