


M. Tech.
FIRST SEMESTER EXAMINATION, 2016-17
ANALOG CMOS DESIGN

[Time: 3 Hours]

[Max. Marks: 100]

Note: Attempt all questions. All question carry equal marks**1.** Attempt any two parts of the following: -**(10x2=20)**

- (a) Determine the small signal gain and the input common mode range (CMR) for the diff-amps shown in Fig 1. Estimate the slew-rate limitations in charging and discharging a 2pF capacitors tied to the outputs of the differential-amps as shown in figure 1

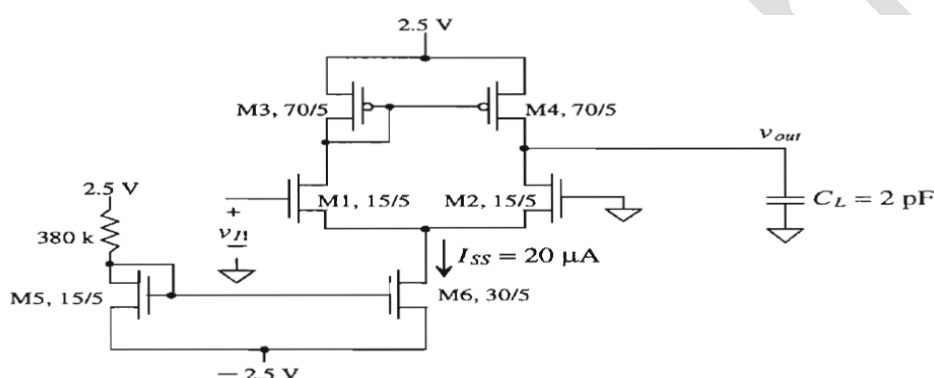**Figure 1**

- (b) Draw a CMOS Op-Amp circuit. Discuss design parameters with characteristic. Explain the circuit analysis on the basis of the following design Parameter (i) Differential Amplifier Bias Current I_{SS} (ii) Selection of the Second stage bias current.
- (c) Draw and analyze the source cross-coupled differential amplifier using MOSFETs. If $I_{SS}=10 \mu A$ and all nMOS have a (15/5) size while all pMOS have a (70/5) size, estimate the maximum difference in potential between the two inputs. Why does this pair not exhibit slew rate limitations?
- 2.** Attempt any four parts of the following:- **(5x4=20)**
- (a) Derive the expressions for the peak current deviation and the times it takes the output current to return to its steady value for simple current mirror (current sink) $V_{DD}= -V_{SS}=2.5V$ and $C_{gd2}=5.7fF, C_{gs1}=C_{gs2}=40fF$. If the step rises very quickly then determine ΔV_{GS} .
- (b) Develop a band gap voltage reference circuit and determine the following: (i) V_{ref} (ii) The conditions under which the TC of the reference is zero.
- (c) Design a 3V reference using the MOSFET only voltage divider assuming $V_{DD}= 5V$ and $V_{SS}=0V$. Determine the temperature coefficient of the reference. Compare the power dissipation when $L_1=L_2=5 \mu m$, $V_{Thn}=0.83 V$, $V_{Thp}=0.91V$, $K_{pn}=50 \mu A/V^2$ and $K_{pp}=17 \mu A/V^2$.
- (d) Design three current sources with values of 10, 20 and $50\mu A$ using n-channel current sink of $10\mu A$. Assume $V_{DD}= -V_{SS}=2.5V$, $V_{GS}=1.2 V$ and length of the devices= $5 \mu m$, $V_{Thn}=0.83 V$, $V_{Thp}=0.91V$, $K_{pn}=50 \mu A/V^2$ and $K_{pp}=17 \mu A/V^2$
- (e) Write a short notes on Switch Capacitor Integrator.
- (f) Design a Double Cascode current sink using $V_{DD}= -V_{SS}=2.5V$ to sink a current of $10\mu A$ and determine the output resistance also

3. Attempt any *two* parts of the following:-

(10x2=20)

- Draw the CMOS configuration of Operational Transconductance Amplifier and discuss its advantages and limitations.
- Design a universal biquad gm-C filter using two identical OTA and determine natural frequency and Q of the filter. Enlist the transfer function for each (i.e LP, HP, BP, BR) configuration.
- Determine the gain and bandwidth of the amplifier as shown in figure 2
 $C_{db1}=5.5\text{fF}$ $C_{gd1}=1.9\text{fF}$ $C'_{ox}=800\text{aF}/\mu\text{m}^2$

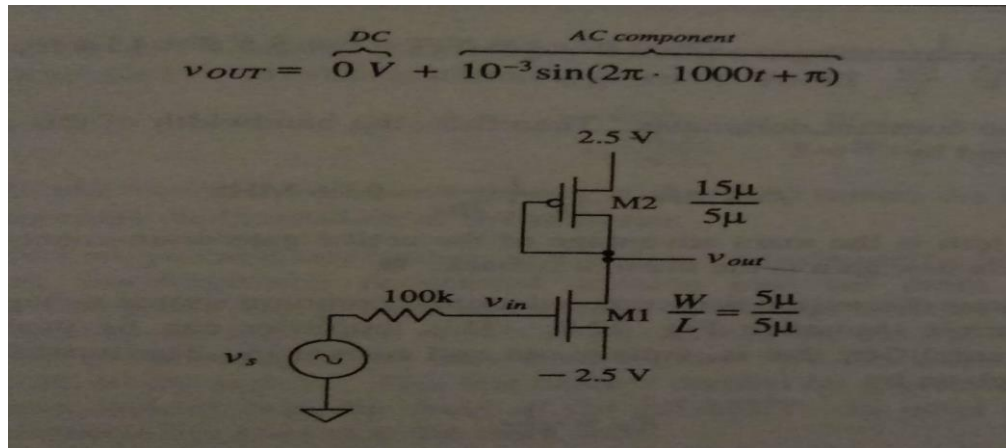


Figure 2

4. Attempt any *four* parts of the following:-

(5x4=20)

- A DAC has a full-scale voltage of 4.97 using a 5V reference, and its minimum output voltage is limited by the value of one LSB. Determine the resolution and dynamic range of the converter.
- Design a 3-bit charge scaling DAC and find the value of the output voltage for $D_2D_1D_0=010$. Assume that $V_{REF}=5\text{V}$ and $C=0.5\text{pF}$
- Draw a block diagram of a Flash ADC and discuss its advantages and limitation
- Perform the operation of a 3-bit successive approximation ADC with $V_{REF}=8$. Make a table that consists of $D_2D_1D_0$, B_2 B_1 B_0 , V_{OUT} and the comparator output, which shows the binary search algorithm of the converter for $V_{IN}=5.5\text{V}$ and 2.5V .
- Draw a small signal model and discuss the frequency response of common source amplifier with active load.
- Design a 3 bit DAC using a R-2R architecture with $R=1\text{k}\Omega$, $R_F=2\text{k}\Omega$ and $V_{REF}=5\text{V}$. Assume that the resistance of the switches are negligible.

5. Attempt any *four* parts of the following: -

(5x4=20)

- Analog CMOS Multiplier
- CMOS Comparator
- Develop a CMOS Wilson current mirror with small signal model circuit and determine the output resistance.
- β multiplier reference self biasing circuit.
- Sensitivity and Temperature Analysis for simple current mirror (Current Sink) circuit.
- Draw a circuit for Cascode differential amplifier and determine the common mode range